


Assignment 9

Manav Garg

7 January 2021

1 Question

Find the output

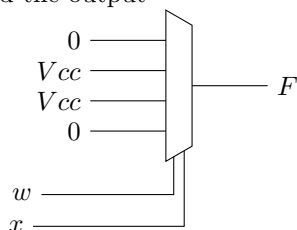

2 Solution

It is a Multiplexer problem So,

w	x	F
0	0	0
0	1	V_{cc}
1	0	V_{cc}
1	1	0

Let's call the output through first multiplexer F

$$F = \bar{w}\bar{x}0 + \bar{w}xV_{cc} + w\bar{x}V_{cc} + wx0$$

here V_{cc} is nothing but 1, so the output through first multiplexer is

$$F = \bar{w}x + w\bar{x}$$

this goes through 2nd multiplexer, So

$$\text{Output } Y = \bar{y}\bar{z}F + \bar{y}zF + y\bar{z}0 + yz0$$

Here F is our output through first multiplexer so

$$Y = (\bar{y}\bar{z} + \bar{y}z)(\bar{w}x + w\bar{x})$$

$$Y = (\bar{y})(\bar{z} + z)(\bar{w}x + w\bar{x})$$

$$Y = \bar{w}x\bar{y} + w\bar{x}\bar{y} \dots \text{as } (\bar{z} + z) = 1$$

y	z	Y
0	0	F
0	1	F
1	0	0
1	1	0

So, final output is $Y = \bar{w}x\bar{y} + w\bar{x}\bar{y}$